

Experiment 1 – Clock and Periodic Signal Generation

Borna
Tavassoli,
810198374

Keywords— Clock, Ring Oscillator, LM555, Schmitt Trigger Oscillator, Frequency Divider, 74HCT, MAXPLUS2, Modelsim, Quartus, LTspice


I. INTRODUCTION

Today, a huge number of circuits depend on their clock inputs and frequency to function properly. In this experiment we deal with 3 different kinds of such clock generators.

Ring Oscillator, LM555 IC (in astable mode) and Schmitt Trigger Oscillator.

II. CLOCK GENERATION USING ICS AND ANALOG COMPONENTS

A. Ring Oscillator

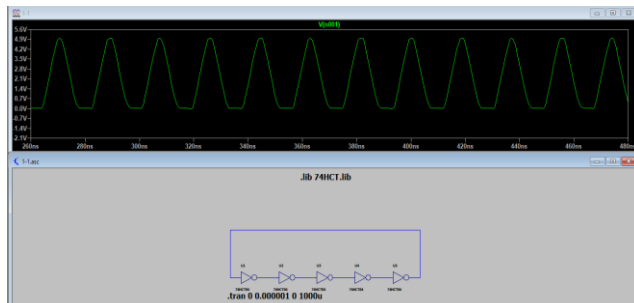

Above is a simulation of a ring oscillator in LTspice using 5 inverters (74HCT04).

$$T = 2N \cdot \text{delay}(\text{inv})$$

And from the picture, we estimate T to be near 20.

So, $20 = 2 \cdot 5 \cdot \text{delay}(\text{inv})$ therefore, $\text{delay}(\text{inv})$ is roughly 2ns.


B. LM555 timer

We can also use an LM555 IC to produce a clock signal. The duty cycle can be modified by changing a resistor value in the circuit. First the timer is tested in astable mode and then 3 different values for R2 are tested and the frequency and duty cycle for each one is calculated.

Note that I have used NE555 IC instead of LM555 since it was not available in my current version of LTspice.

Note that the capacitors are all 10nF and $R1 = 1 \text{ K}\Omega$

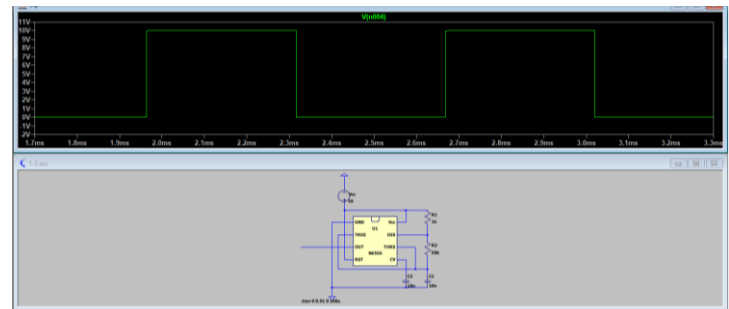- For the first part we have simply implemented LM555 with the following values
 $R1 = 1 \text{ K}\Omega$, $R2 = 50 \text{ K}\Omega$
 $T = 0.693 \times (1 + 100) \times 10^{-3} \times 10 \times 10^{-9} = 0.69 \text{ ms}$
 $f = 1 / T = 1.44 \text{ kHz}$
Duty Cycle = 50.49%



2.1.

$$R1 = 1 \text{ K}\Omega, R2 = 1 \text{ K}\Omega$$

$$T = 0.693 \times (1 + 2) \times 10^{-3} \times 10 \times 10^{-9} = 0.02 \text{ ms}$$

$$f = 1 / T = 0.05 \text{ MHz}$$

$$\text{Duty Cycle} = 66.66\%$$

2.2.

$$R1 = 1 \text{ K}\Omega, R2 = 10 \text{ K}\Omega$$

$$T = 0.693 \times (1 + 20) \times 10^{-3} \times 10 \times 10^{-9} = 0.14 \text{ ms}$$

$$f = 1 / T = 0.07 \text{ MHz}$$

$$\text{Duty Cycle} = 52.49\%$$

2.3.

$$R1 = 1 \text{ K}\Omega, R2 = 100 \text{ K}\Omega$$

$$T = 0.693 \times (1 + 200) \times 10^{-3} \times 10 \times 10^{-9} = 1.39 \text{ ms}$$


$$f = 1 / T = 0.007 \text{ MHz}$$

$$\text{Duty Cycle} = 50.2\%$$

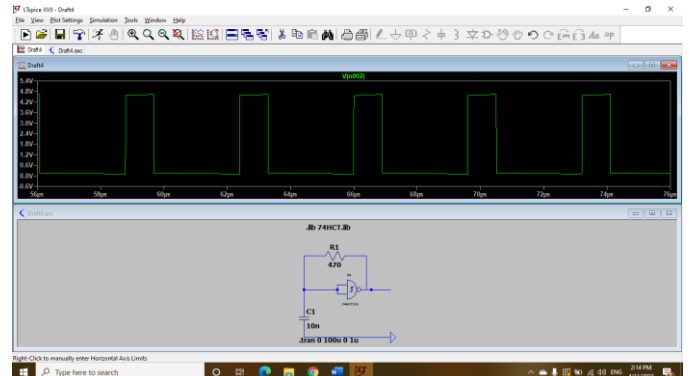C. Schmitt trigger oscillator

Note that we have used a 74HCT14 in our circuit.

$$f = \alpha / RC \Rightarrow \alpha = RC / T$$




- $R = 470 \Omega$, $dx = 0.004 \text{ ms} \Rightarrow \alpha = 1.175$
- $R = 1 \Omega$, $dx = 0.007 \text{ ms} \Rightarrow \alpha = 1.42$
- $R = 2.2 \Omega$, $dx = 0.015 \text{ ms} \Rightarrow \alpha = 1.46$

III. FPGA DESIGN

 
A. Ring Oscillator

We redo the ring oscillator part now in Verilog. If we run the testbench the result is as follows:




As we had expected, $T = 20\text{ns}$. So, the frequency is $1/T = 5 \cdot 10^7\text{Hz}$.

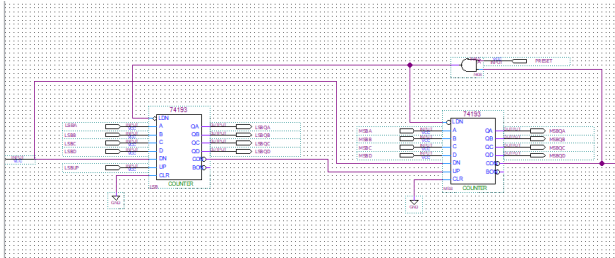
B. Synchronous Counter as a Frequency Divider




As shown in the picture above, we have used two cascaded blocks of 74193 IC with a pre-setting mechanism. When the 4-bit LSB counters reaches 1111, the MSB is incremented by 1. Parallel loading is used to start the counting with 10001110; So, it takes $255 - 142 (10001110) = 113$ clock cycles for out to iterate a full cycle and then its value becomes 10001110. As you can see the duty cycle is very little!

 

C. T Flip Flop

 


 Now that we've used a TFF, the duty cycle will be 50% as shown below:




A. Automatic Baud Rate Calculator


First, we need to draw the controller:

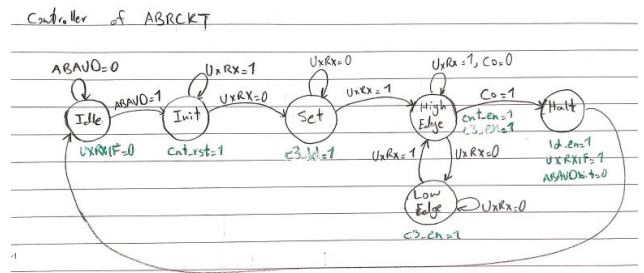

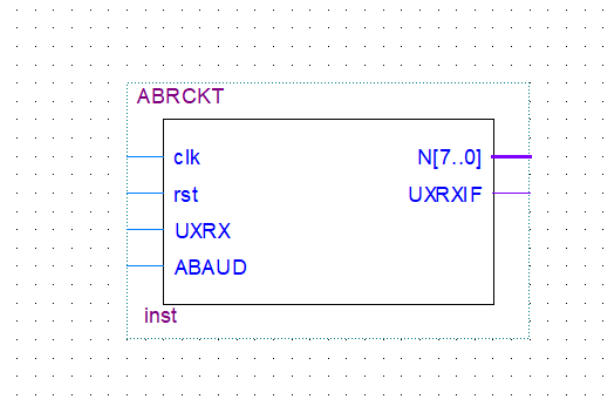
Then we implement the controller along with its data path to generate ABRCKT:



 Now using the said component, we synthesis BRGCKT as shown below:



 If we test the newly built circuit, we notice that the frequencies are quite similar!



Note that:

$$t1 = 3118180, t2 = 9046180 \Rightarrow dt = 5928000\text{ps}$$

$$\Rightarrow F_{BRGCKT} = 168,690$$

$$T = 2 \cdot 2 \cdot 3 = 12 \cdot 10^{-9}, N = 28 \Rightarrow F_T = 10^9 / (12 \cdot 2 \cdot 228) = 182,748 \text{ which has about 8 percent error.}$$

IV. BAUD RATE GENERATOR FOR UART SERIAL COMMUNICATION

V. CONCLUSION

Having done these experiments, we have learned to use not only regular clock, but also, custom made clocks for different purposes. We were able to build a Ring Oscillator and use it to build Frequency Dividers, and later on, Baud Rate generators. We also got familiarized with UART and its different implementations.